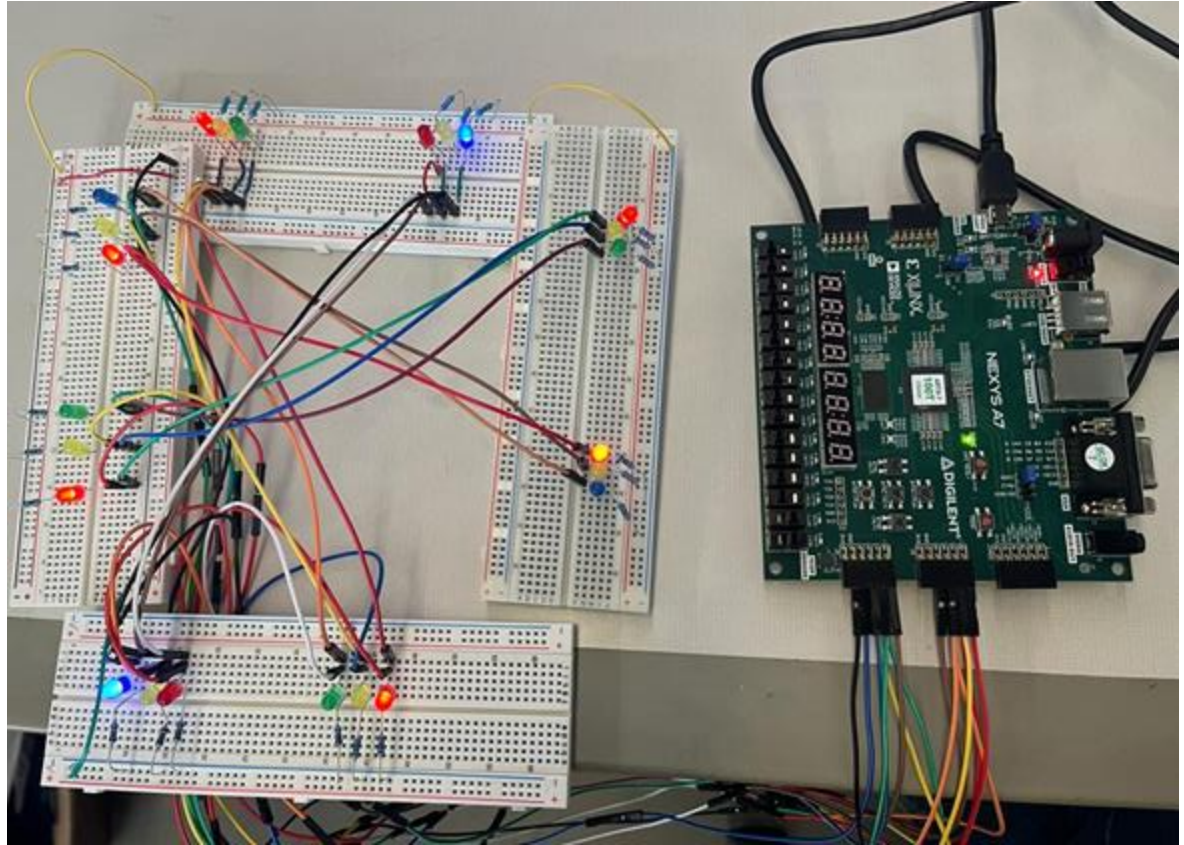# 4-Way Traffic Light

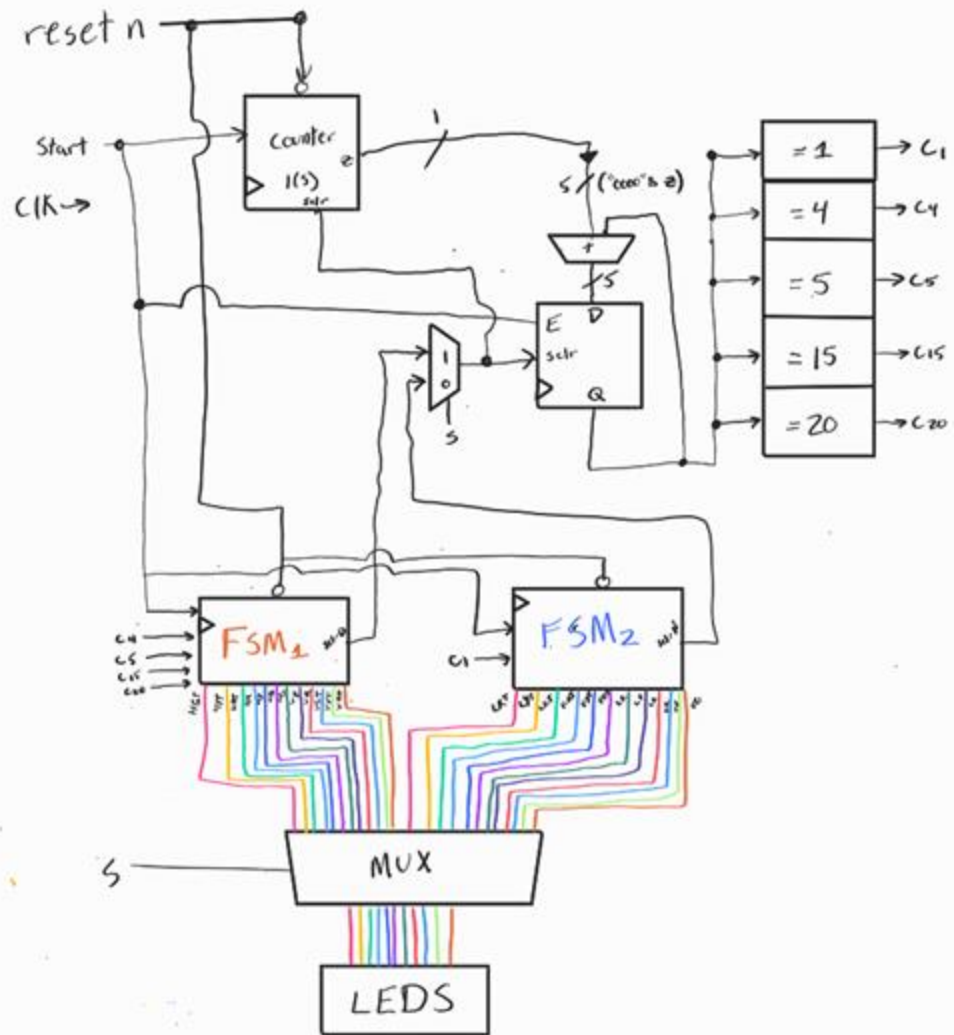By: Nolan Mittison and Davio Mazzella

How it works
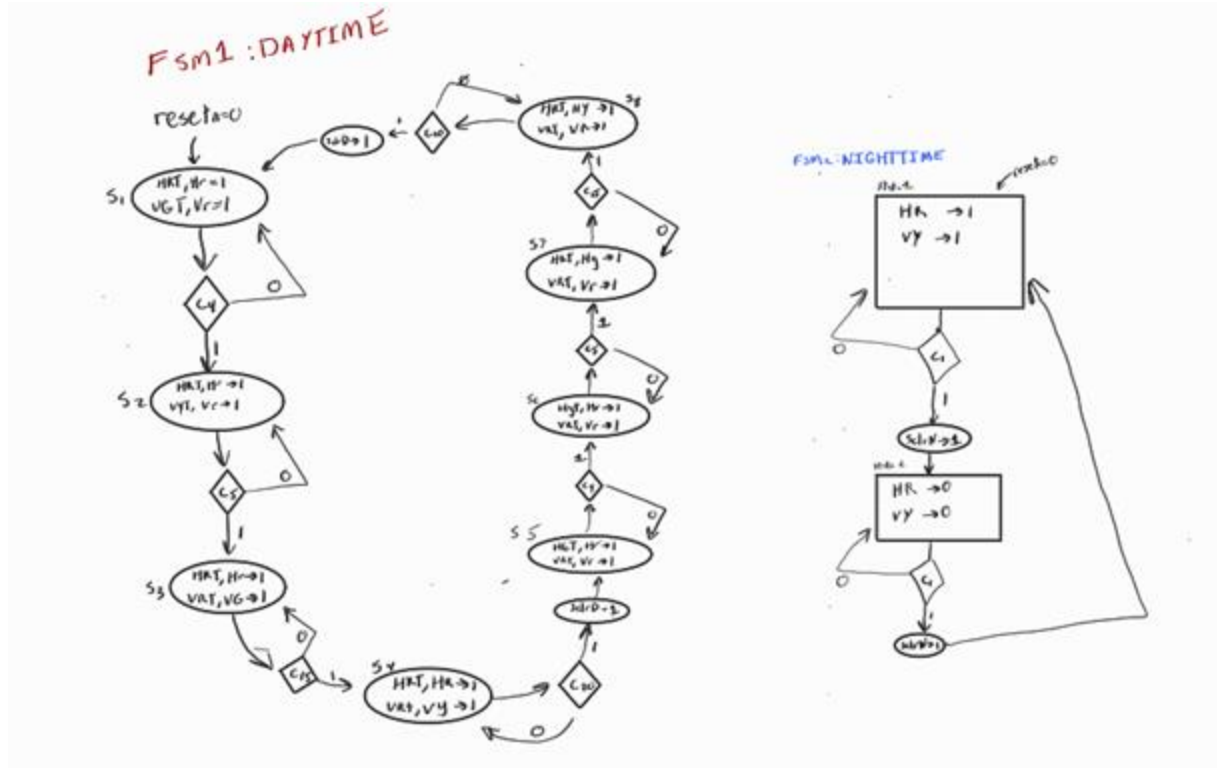
- Clock Intervals
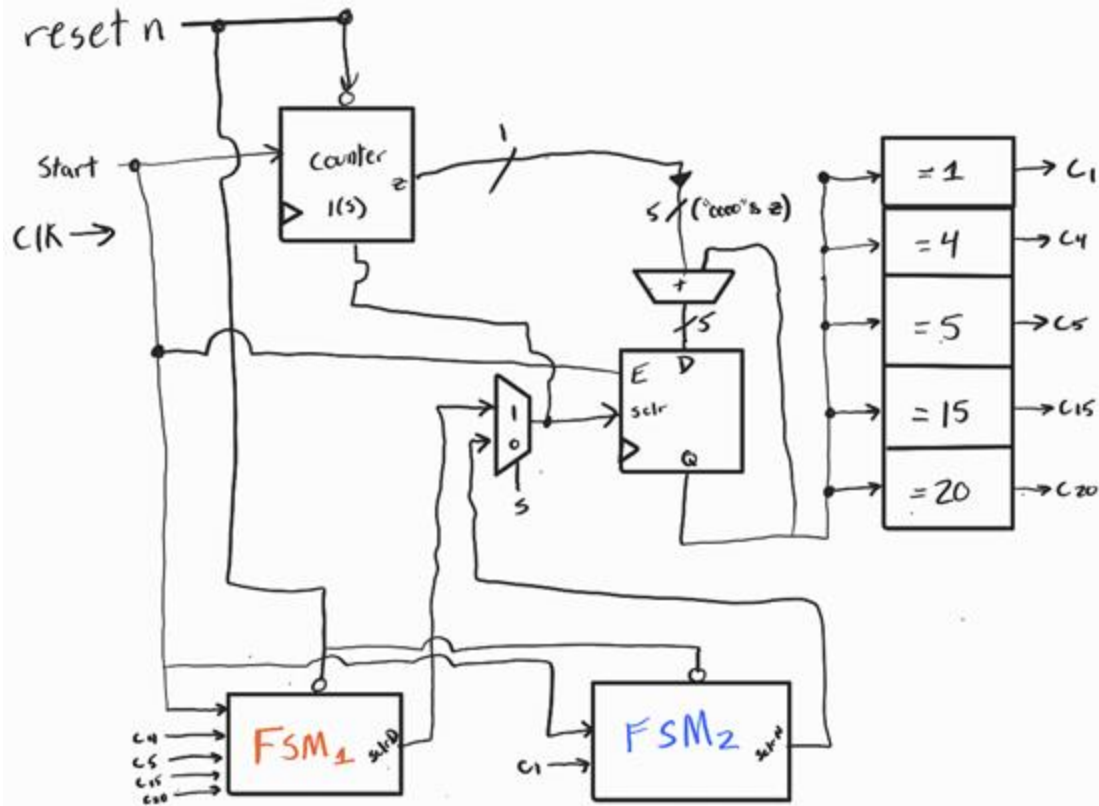
- Day/Night Cycle

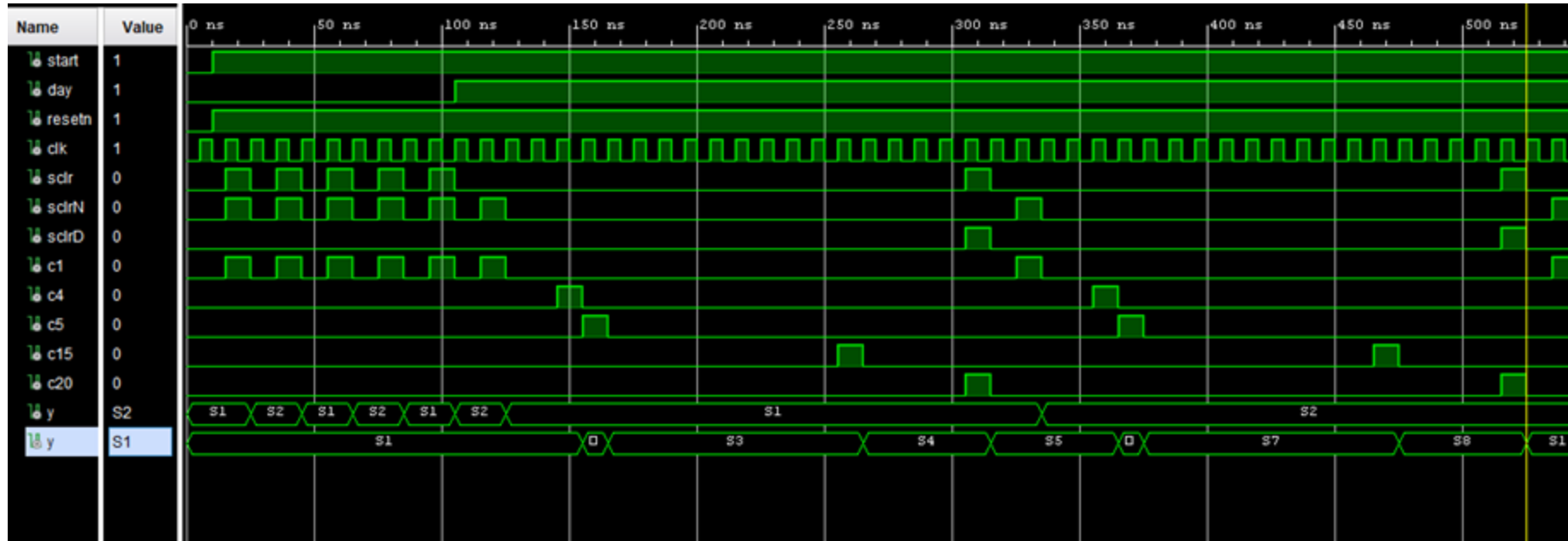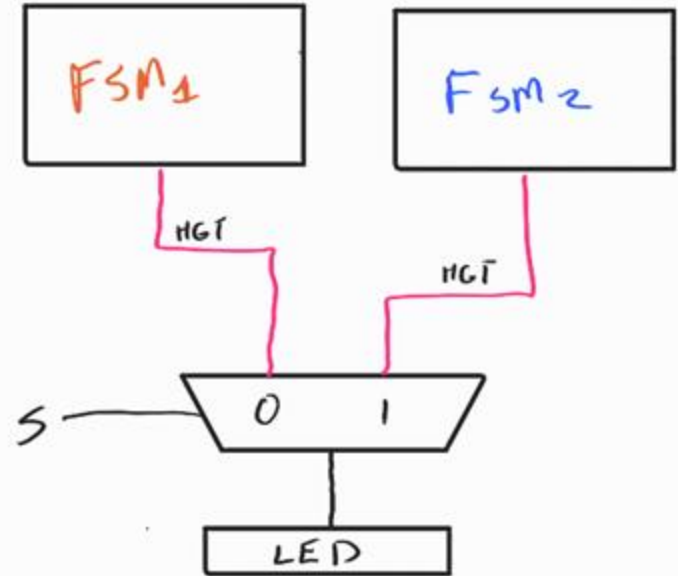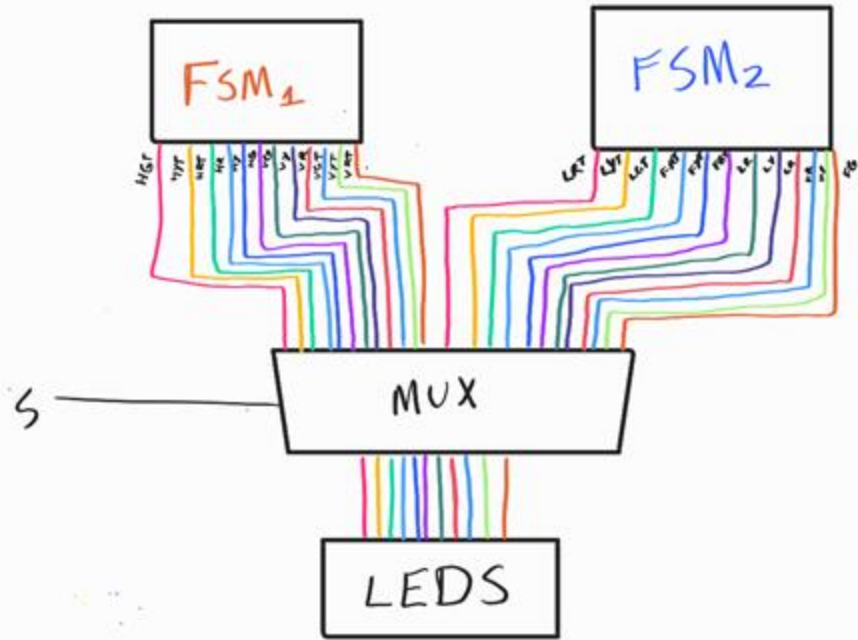- LED Display

Block Diagram

Finite State Machines

Clocks and Timers

Clocks and Timers Simulation

Multiplexers

Demo