DESIGN PROJECT

DIGITAL LOGIC DESIGN
ECE-2700

Caleb Bacon
Suha Eshaq
Wissam Isaac
Cody Wilson

DECIMAL TO BINARY CONVERTER

- A user will be able to select any decimal number in the range of 0 – 9999 that will be displayed on the four-seven segment displays on the Basys 3 board.
- Have the ability to switch between ones, tens, hundreds and thousands place using right and left buttons.
- A user will have a range of 0-9 for each place using up and down button on each seven segment display.
- Finally, the result of binary number will be represented through the LEDs on the Basys 3 board.

LEFT AND RIGHT BUTTONS

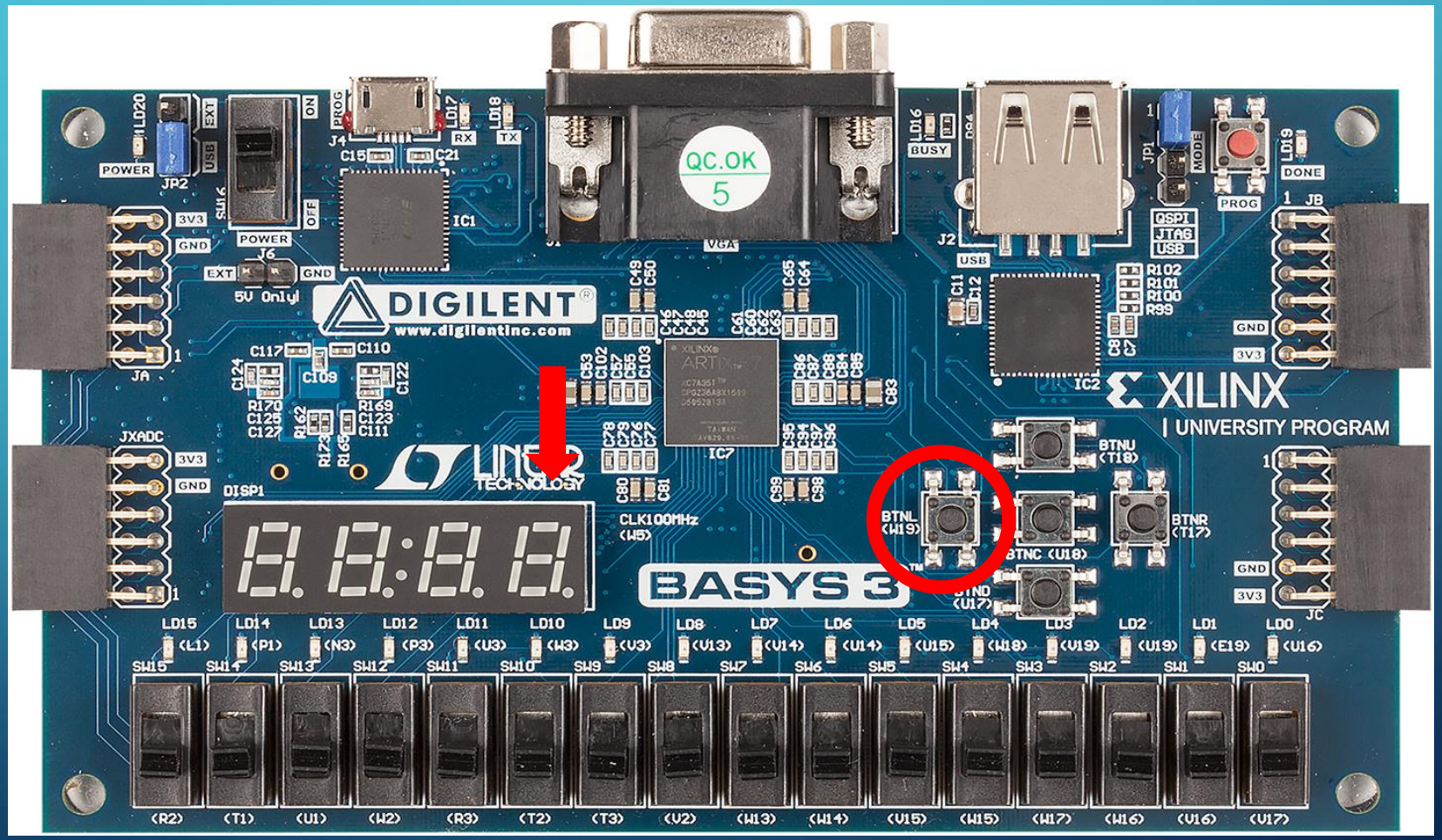

LEFT AND RIGHT BUTTONS

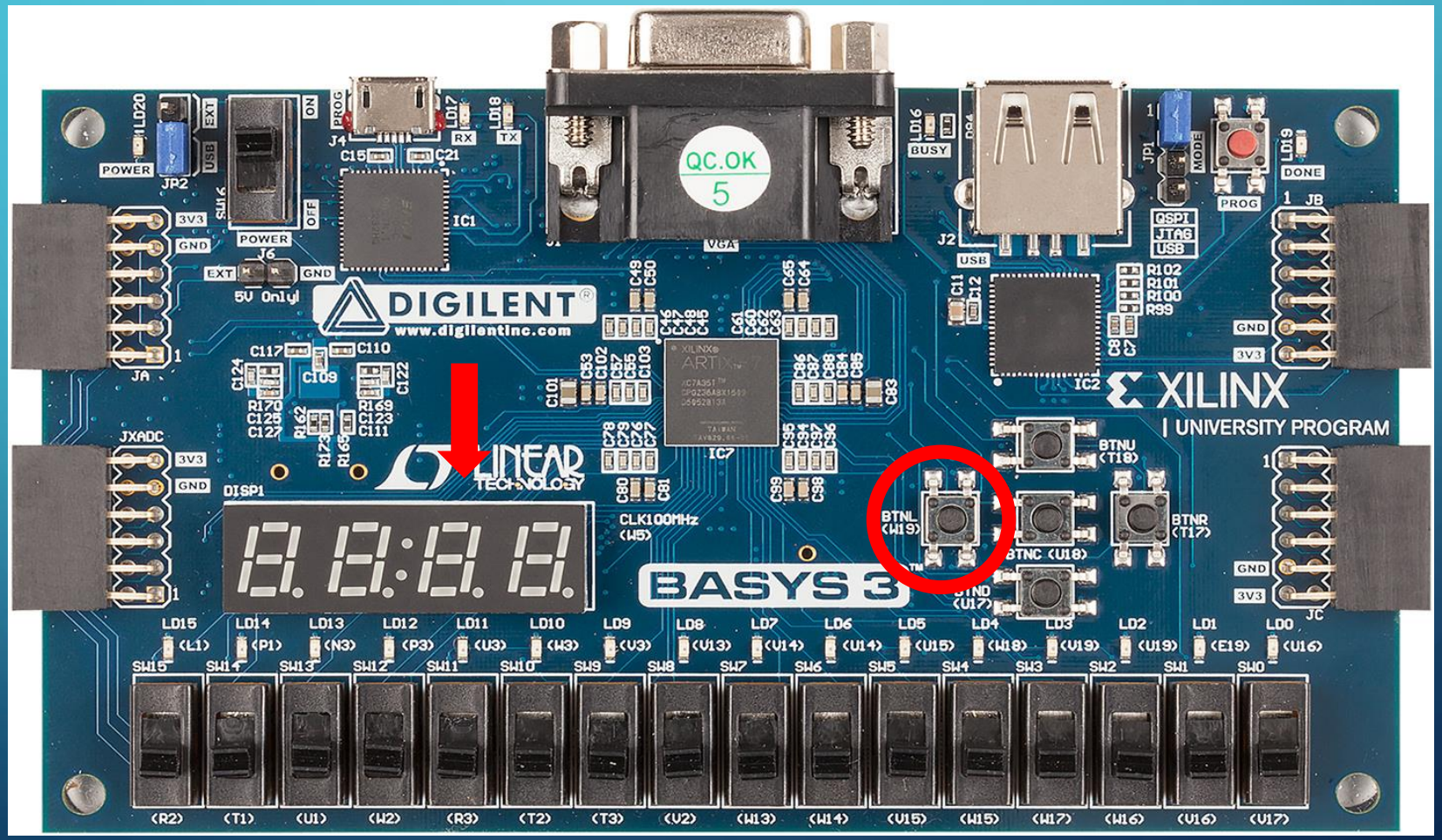

LEFT AND RIGHT BUTTONS

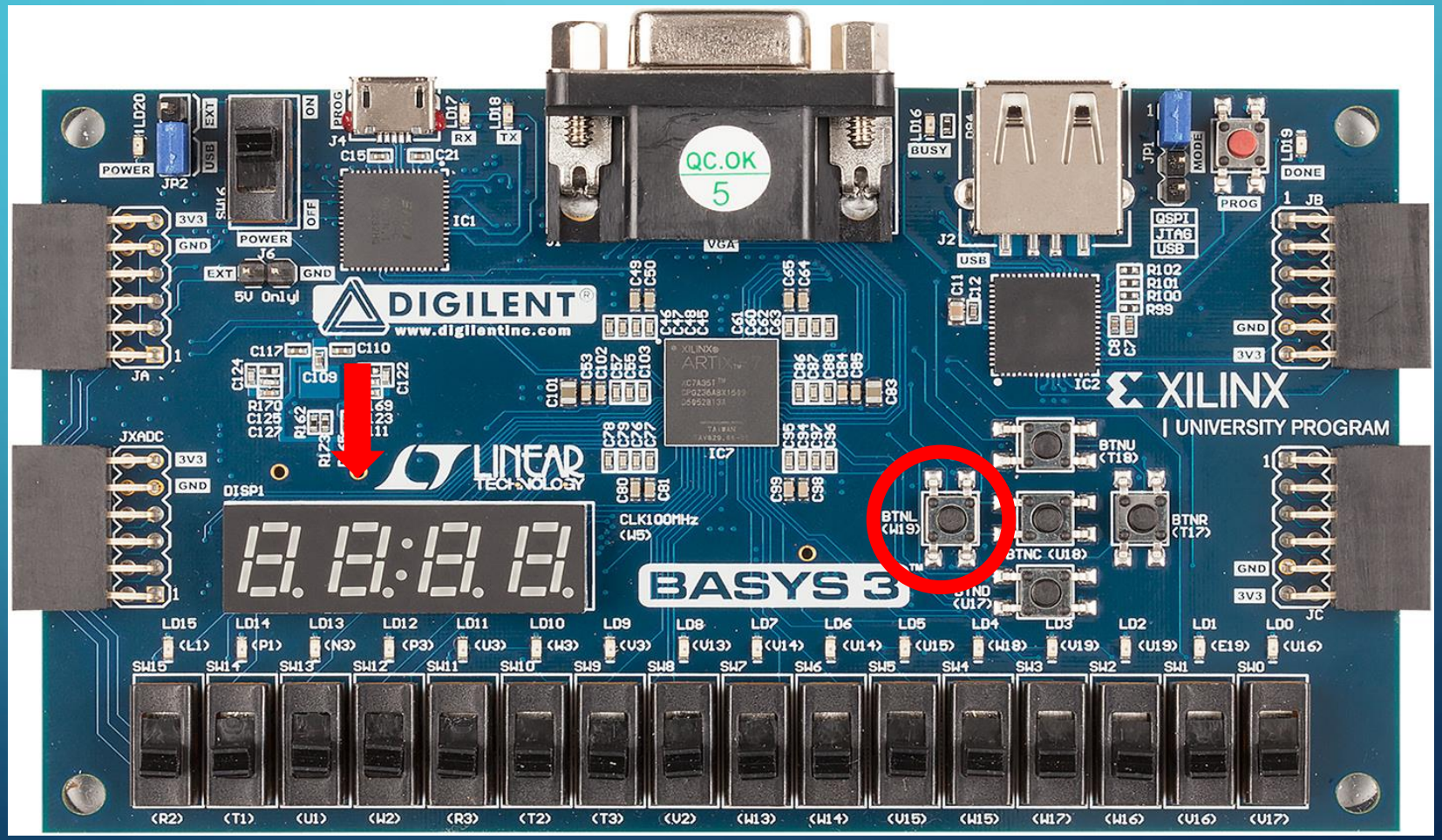

LEFT AND RIGHT BUTTONS

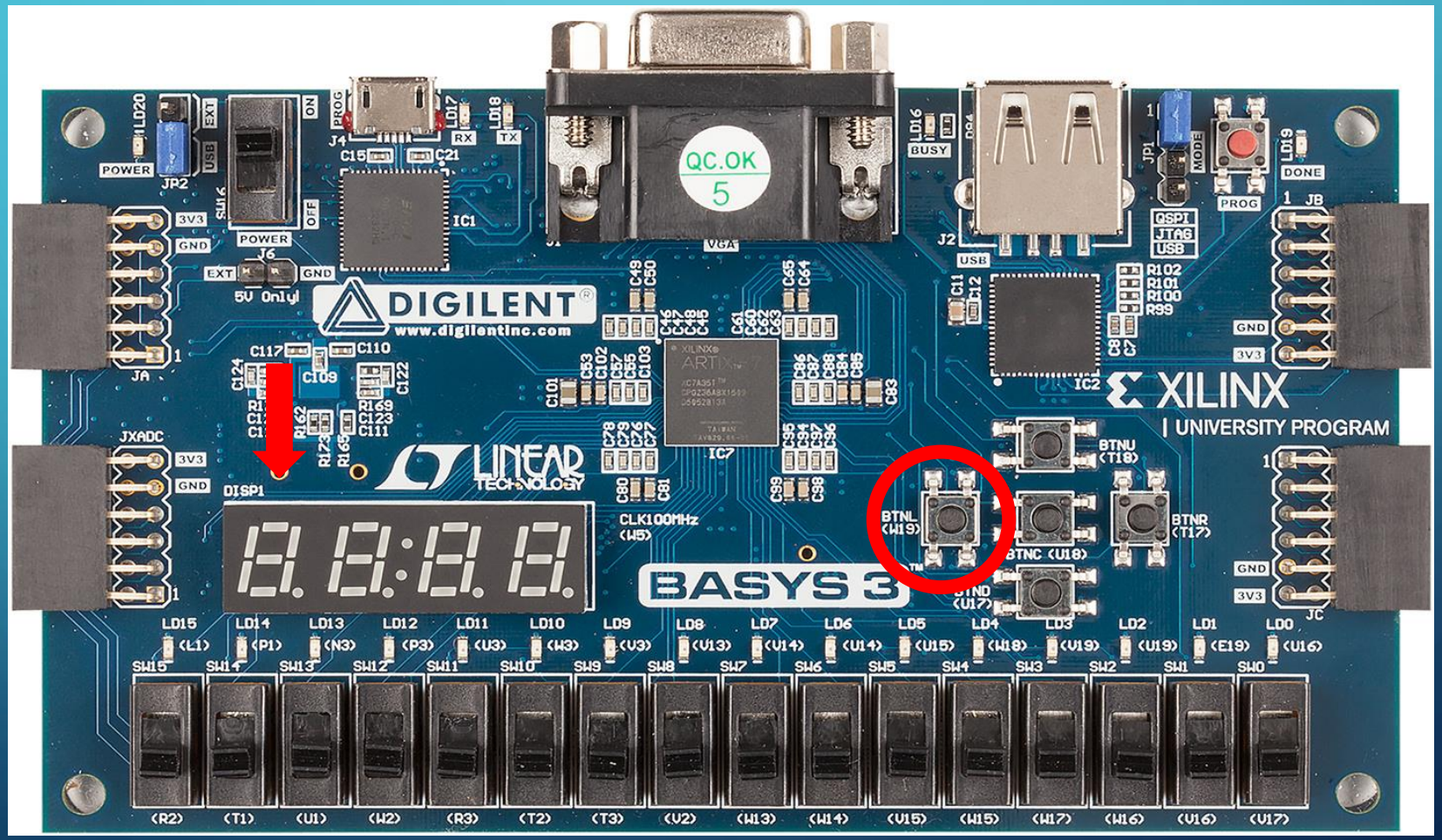

LEFT AND RIGHT BUTTONS

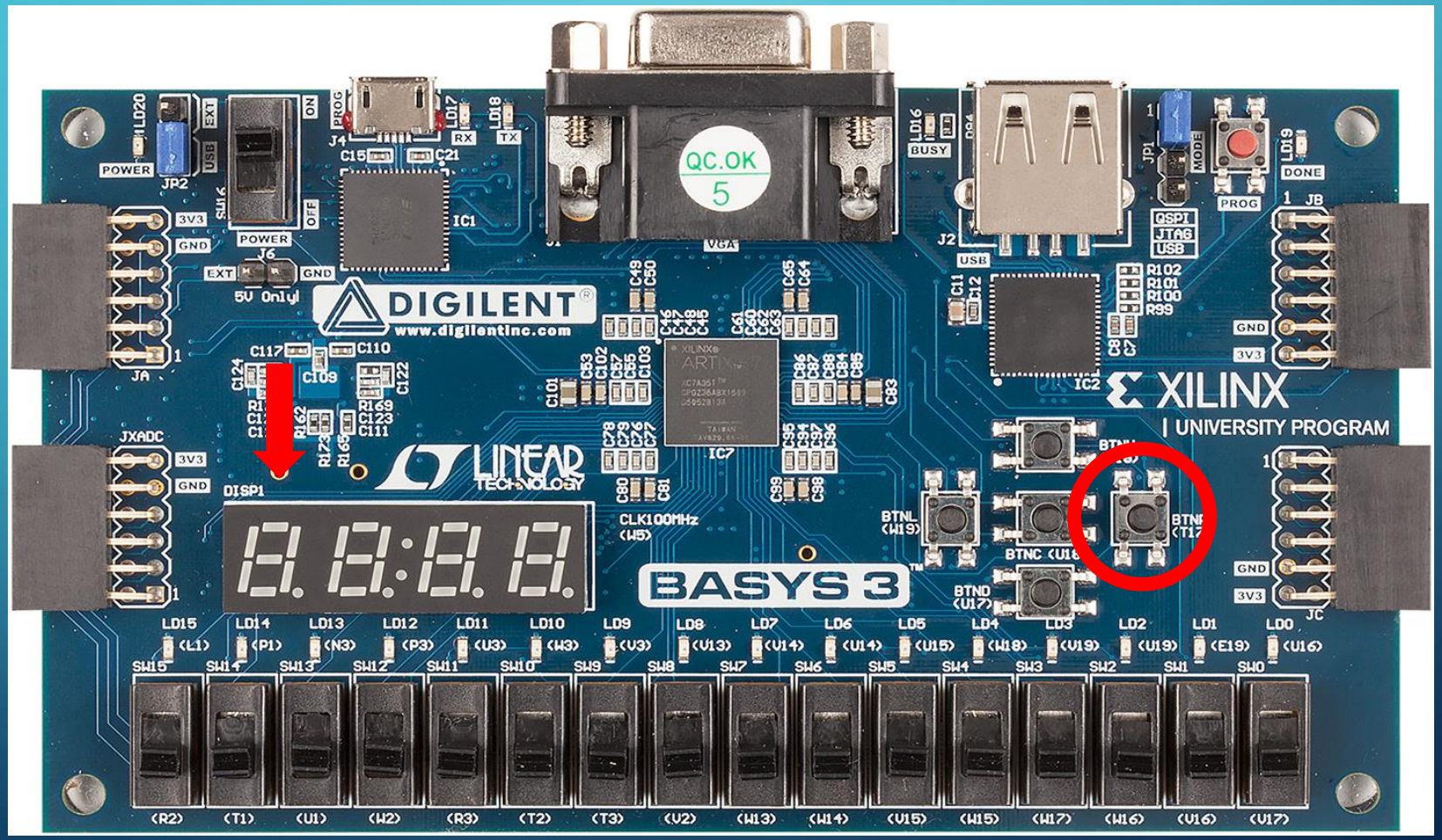

LEFT AND RIGHT BUTTONS

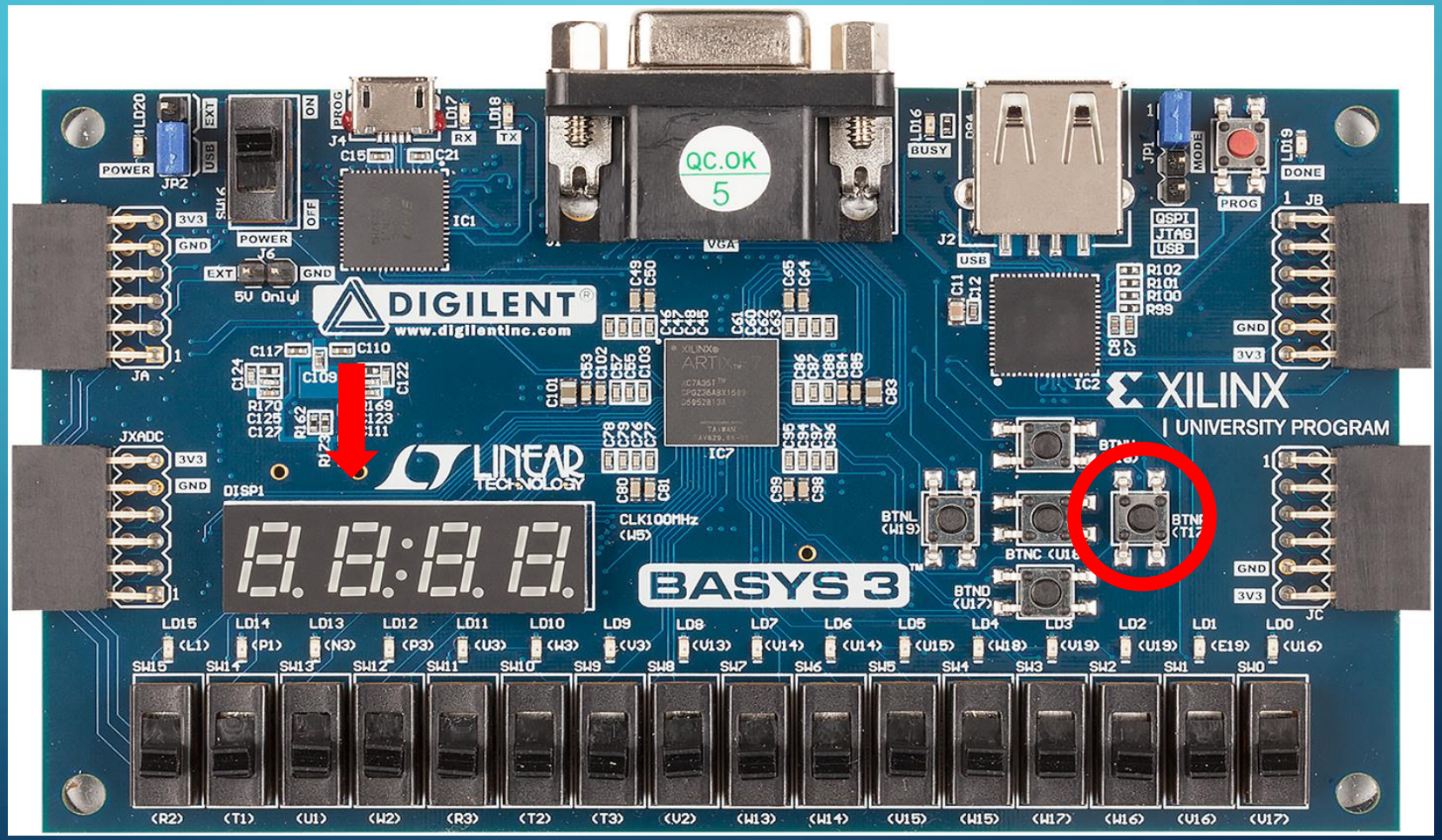

LEFT AND RIGHT BUTTONS

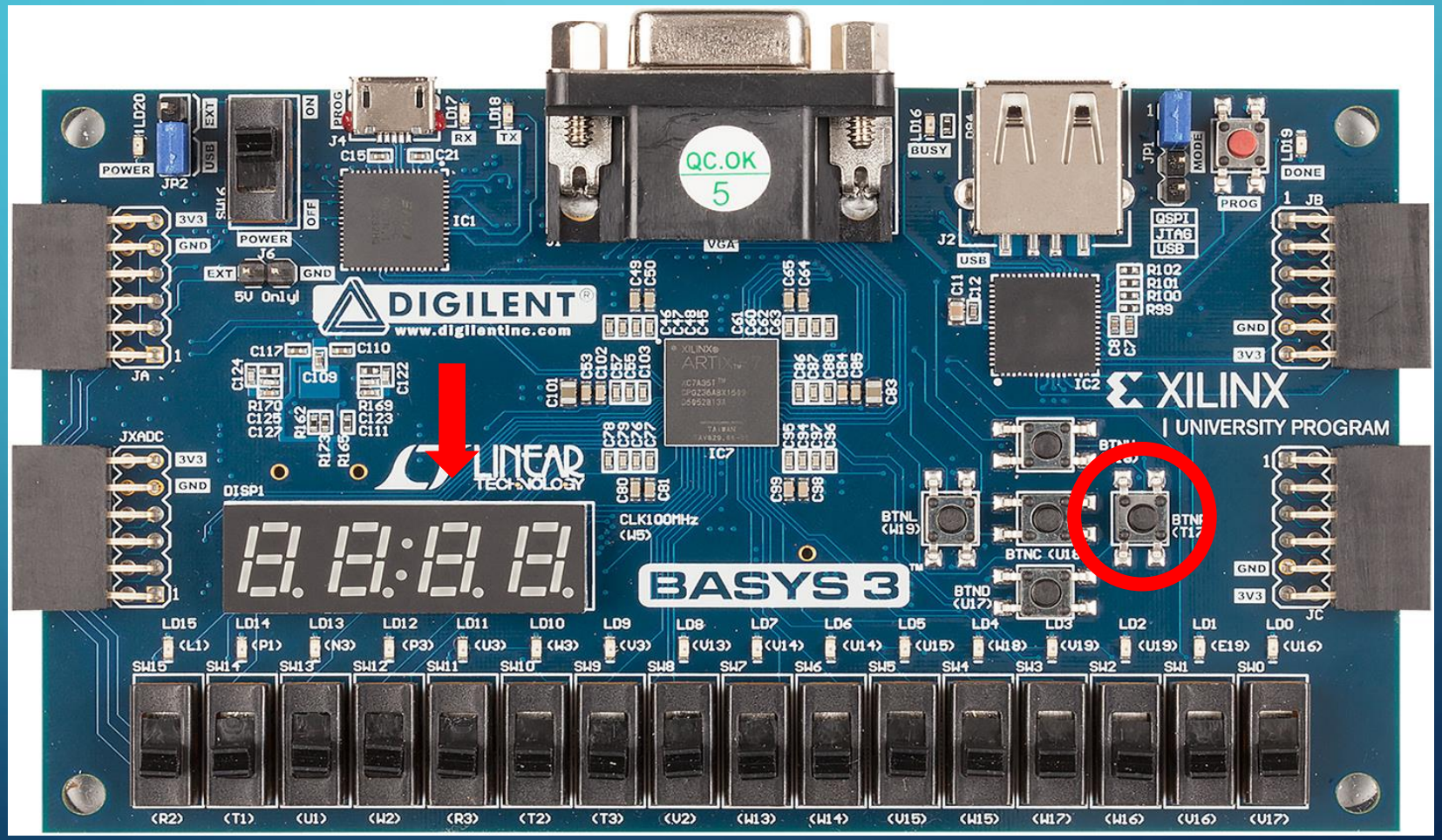

LEFT AND RIGHT BUTTONS

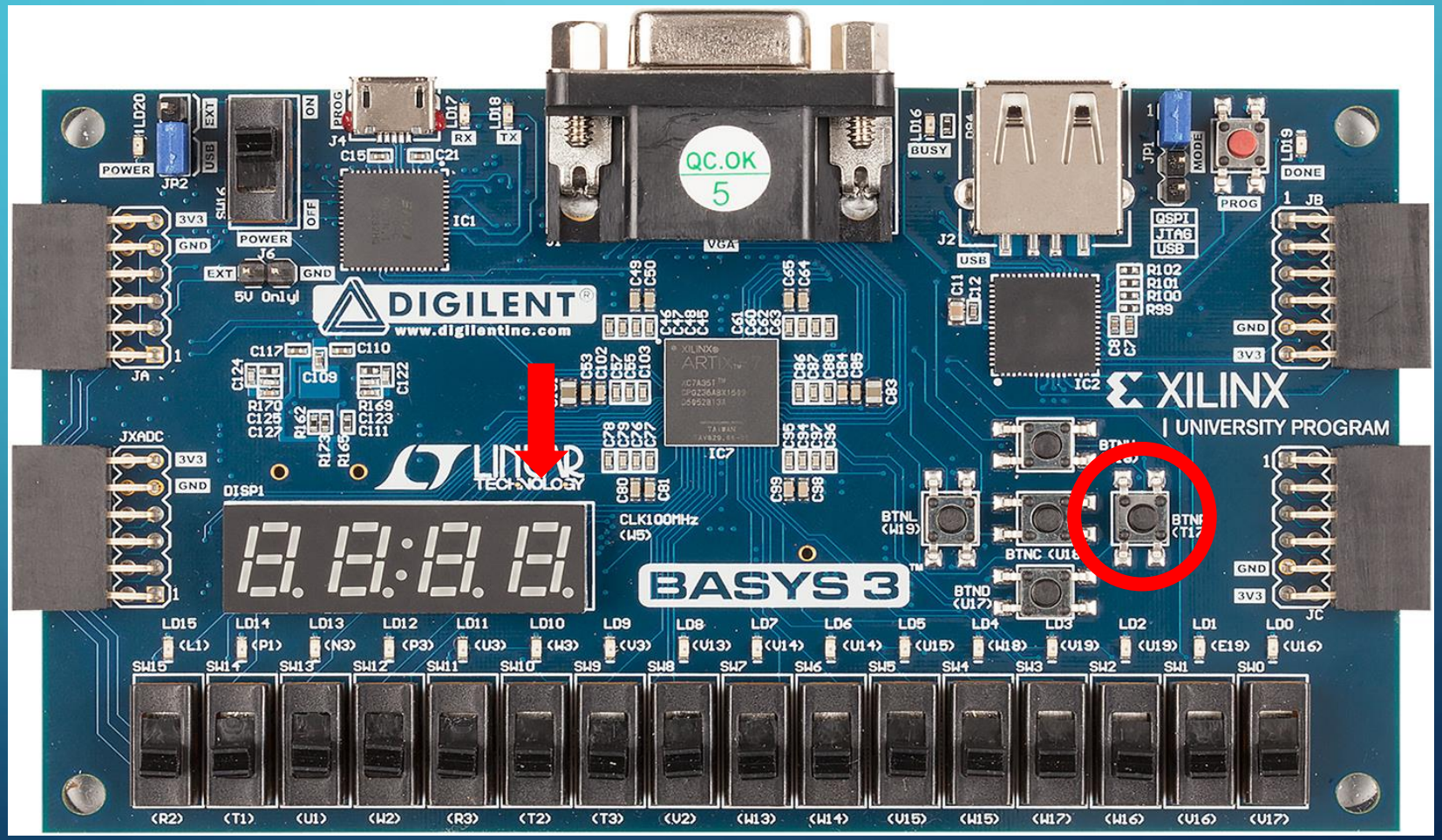

UP AND DOWN BUTTONS

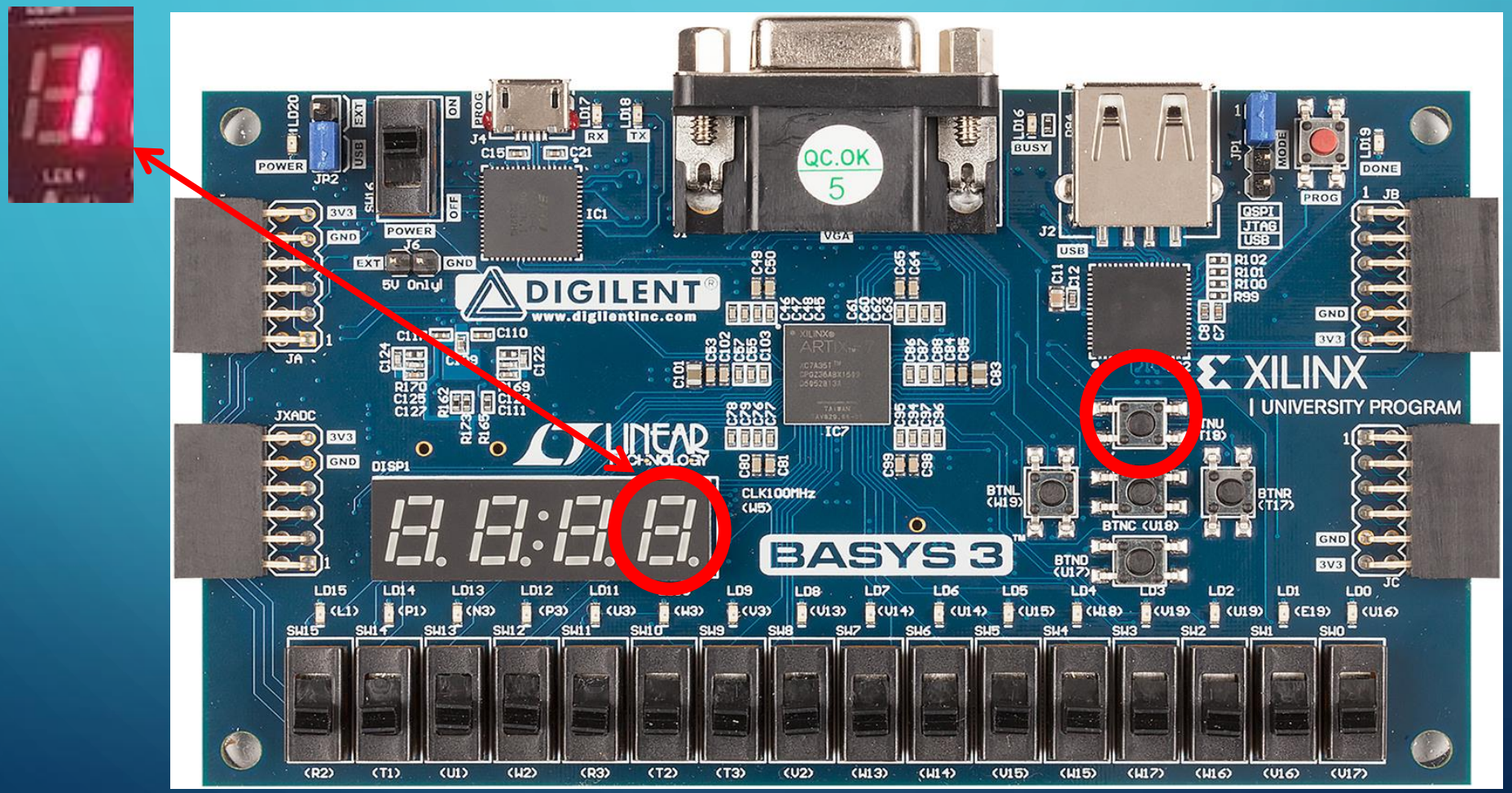

UP AND DOWN BUTTONS

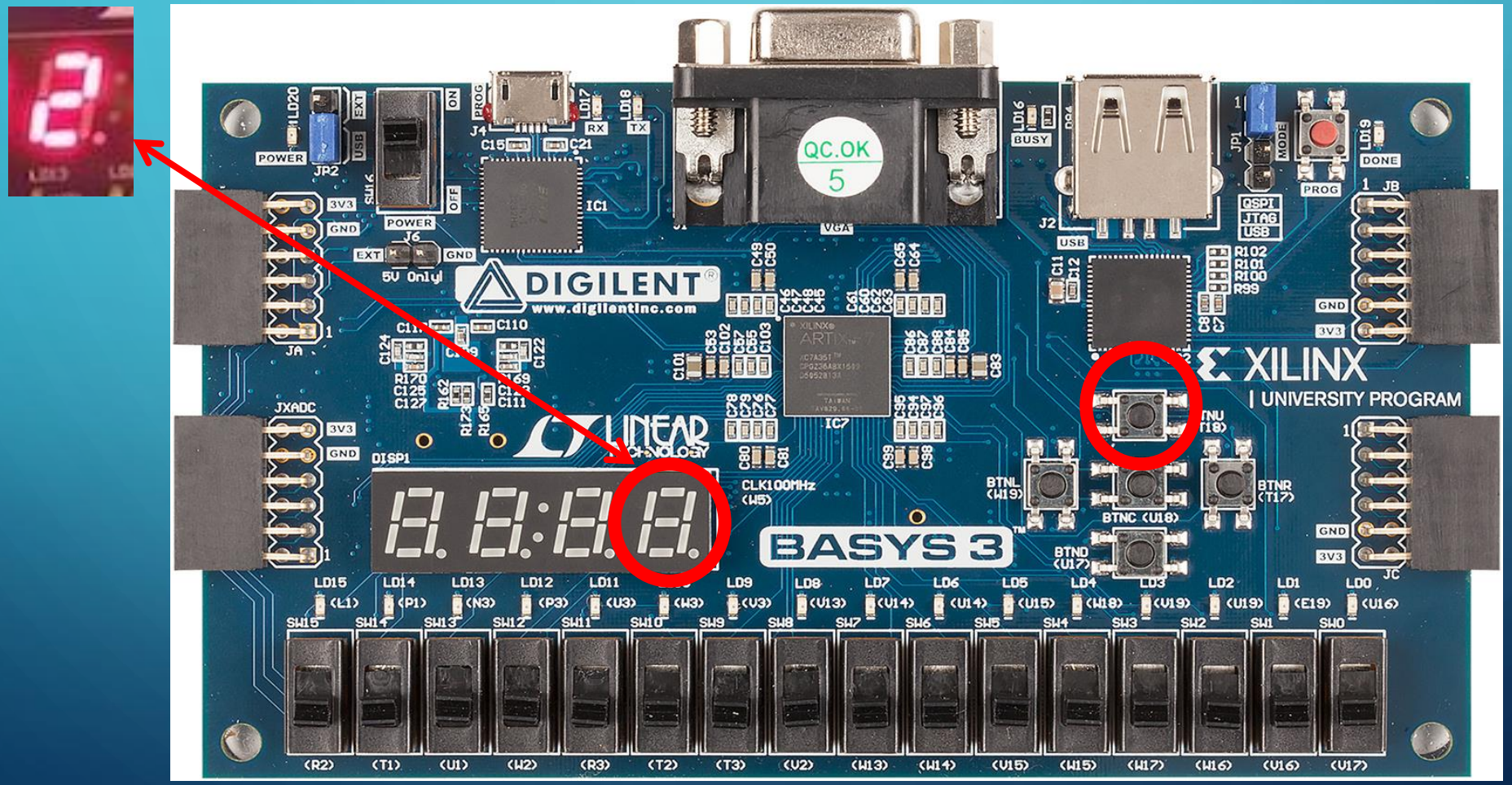

UP AND DOWN BUTTONS

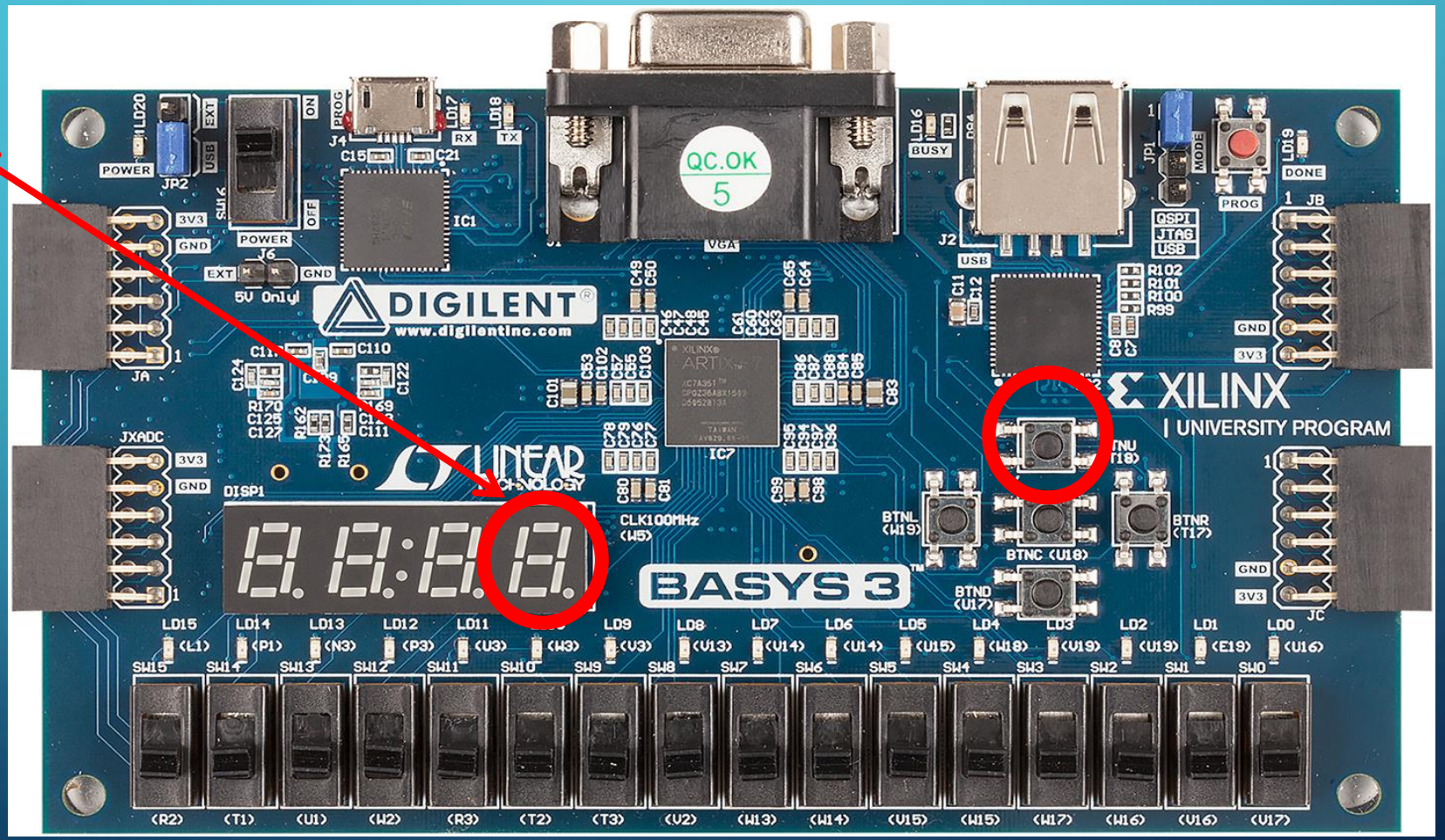

UP AND DOWN BUTTONS

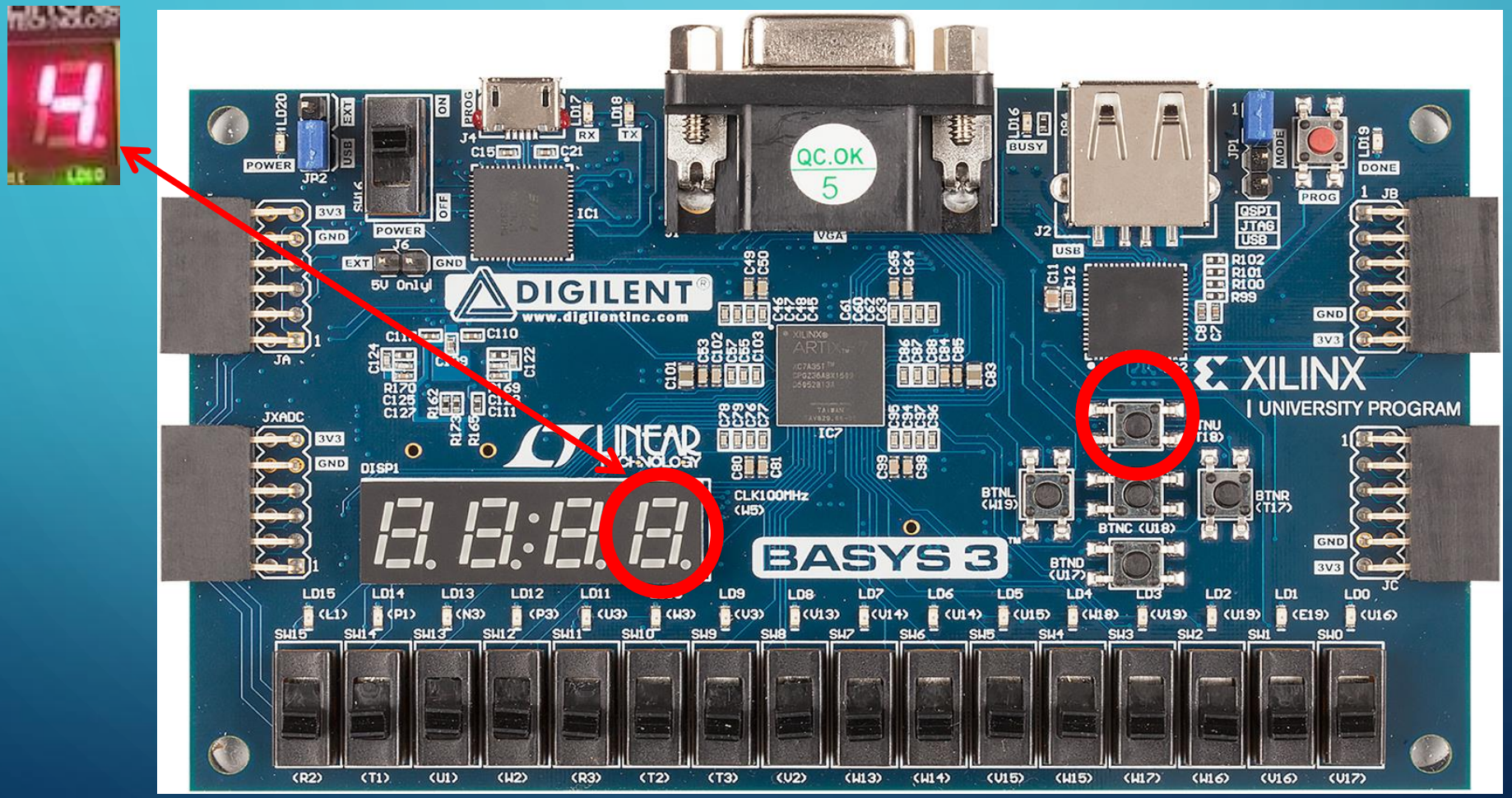

UP AND DOWN BUTTONS

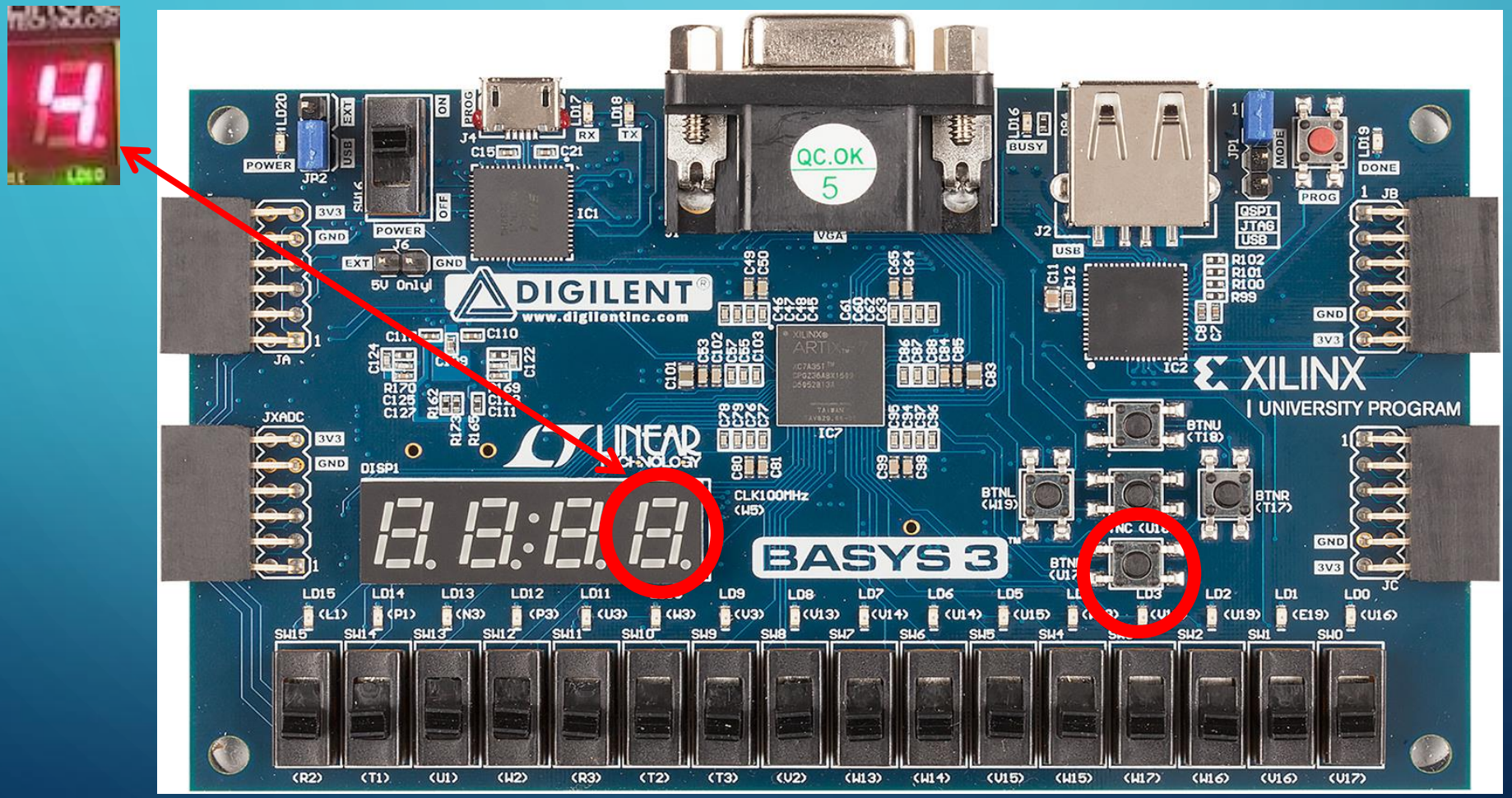

UP AND DOWN BUTTONS

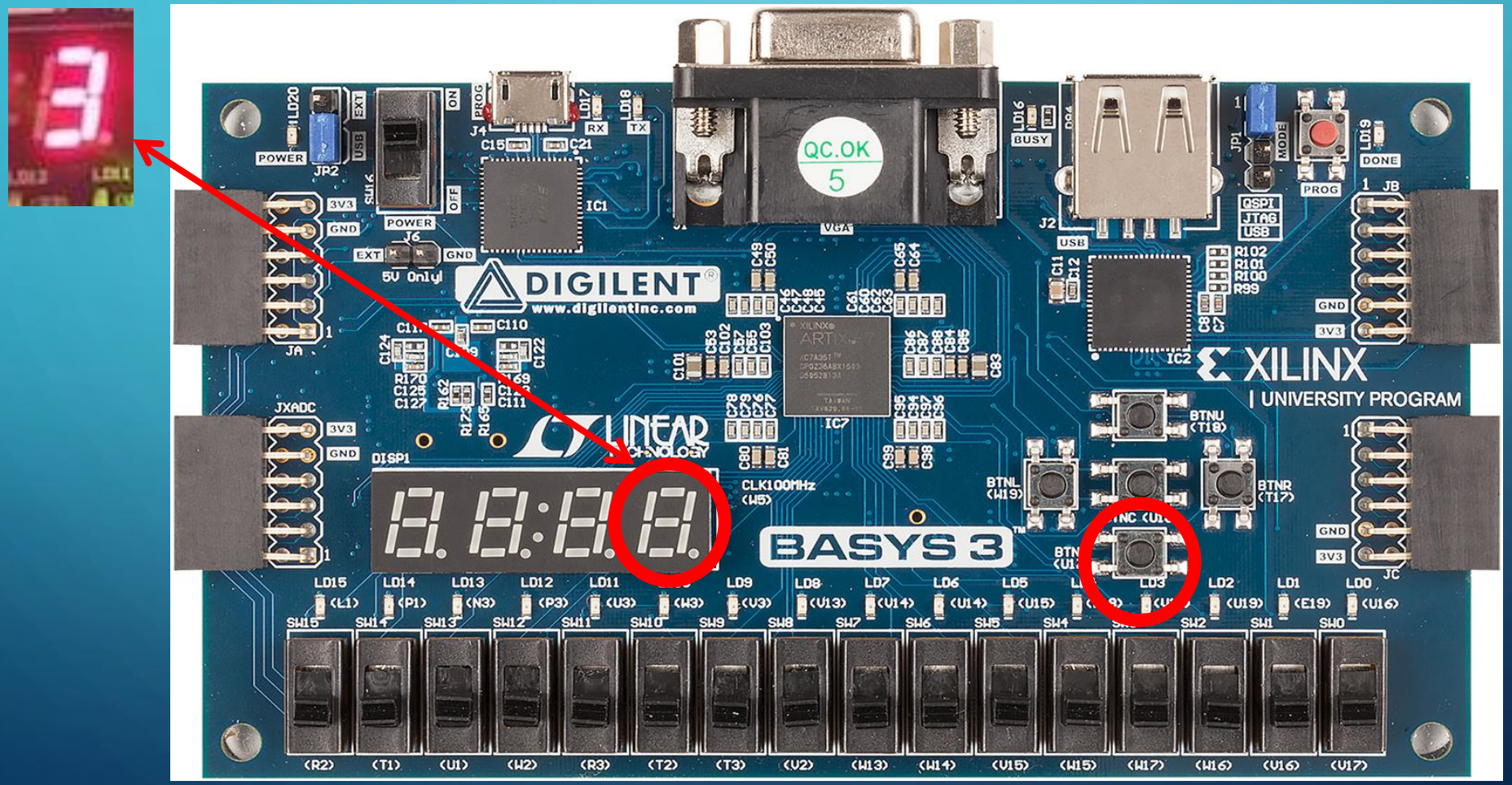

UP AND DOWN BUTTONS

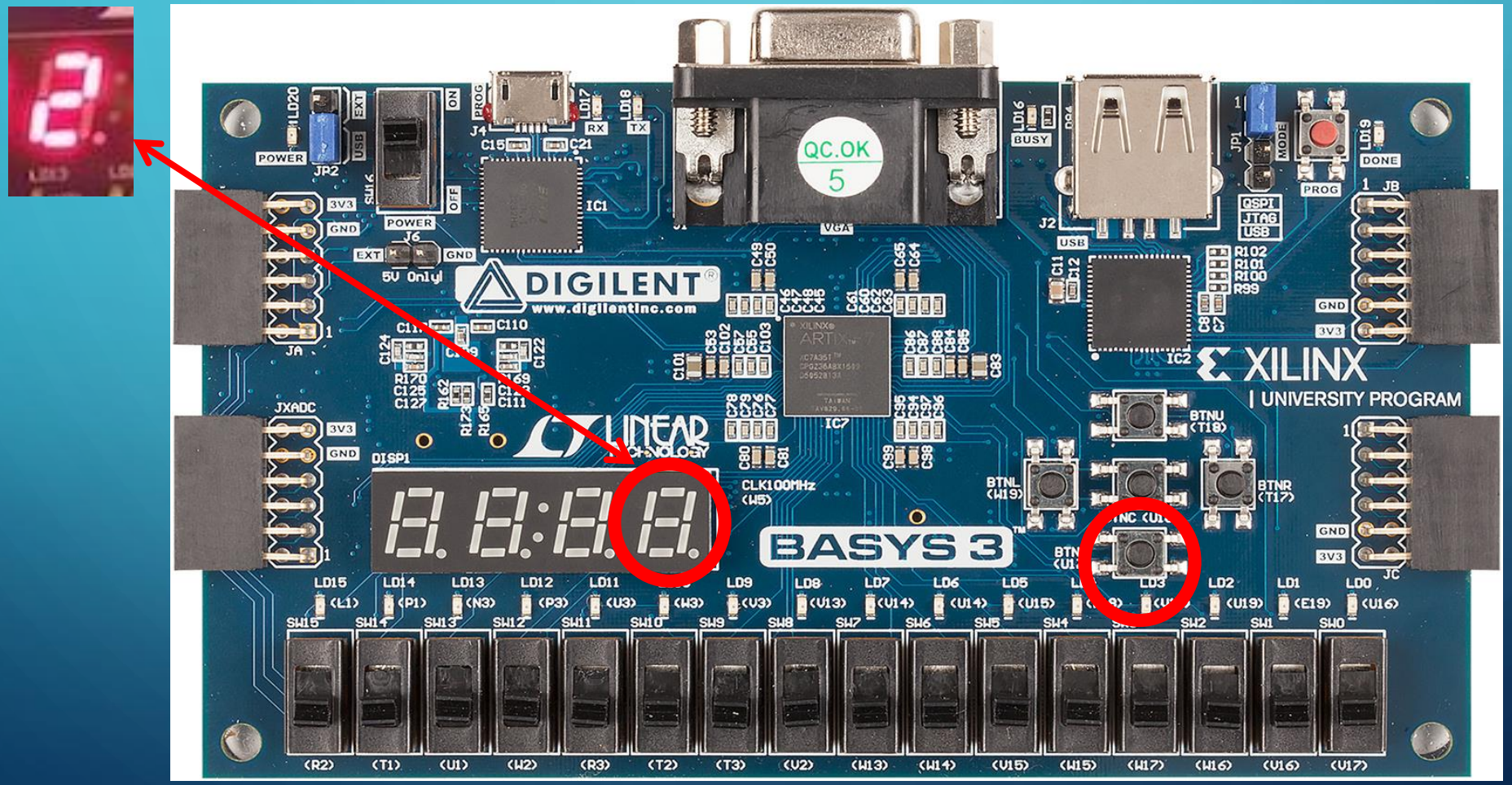

UP AND DOWN BUTTONS

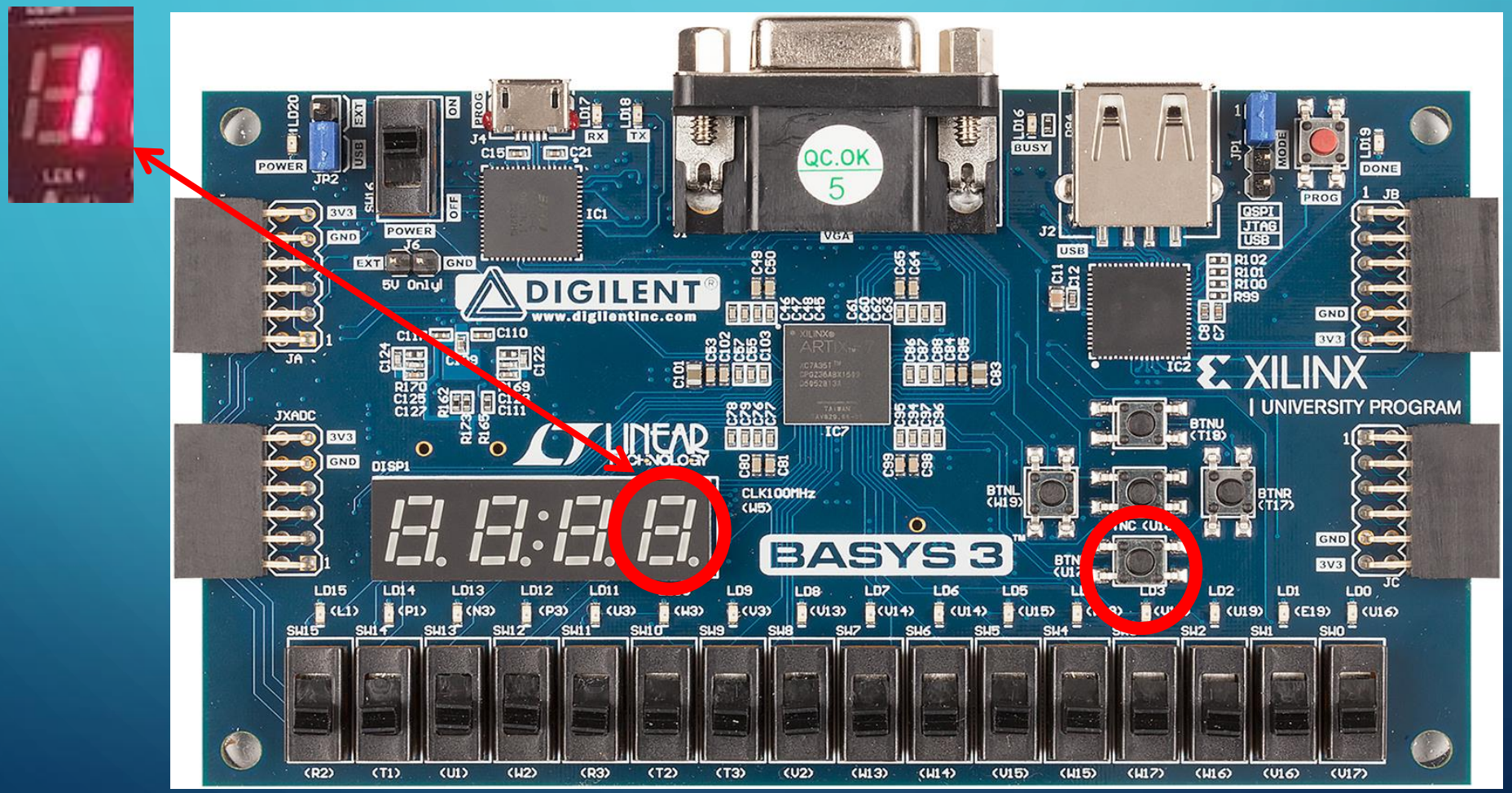

RESET BUTTON

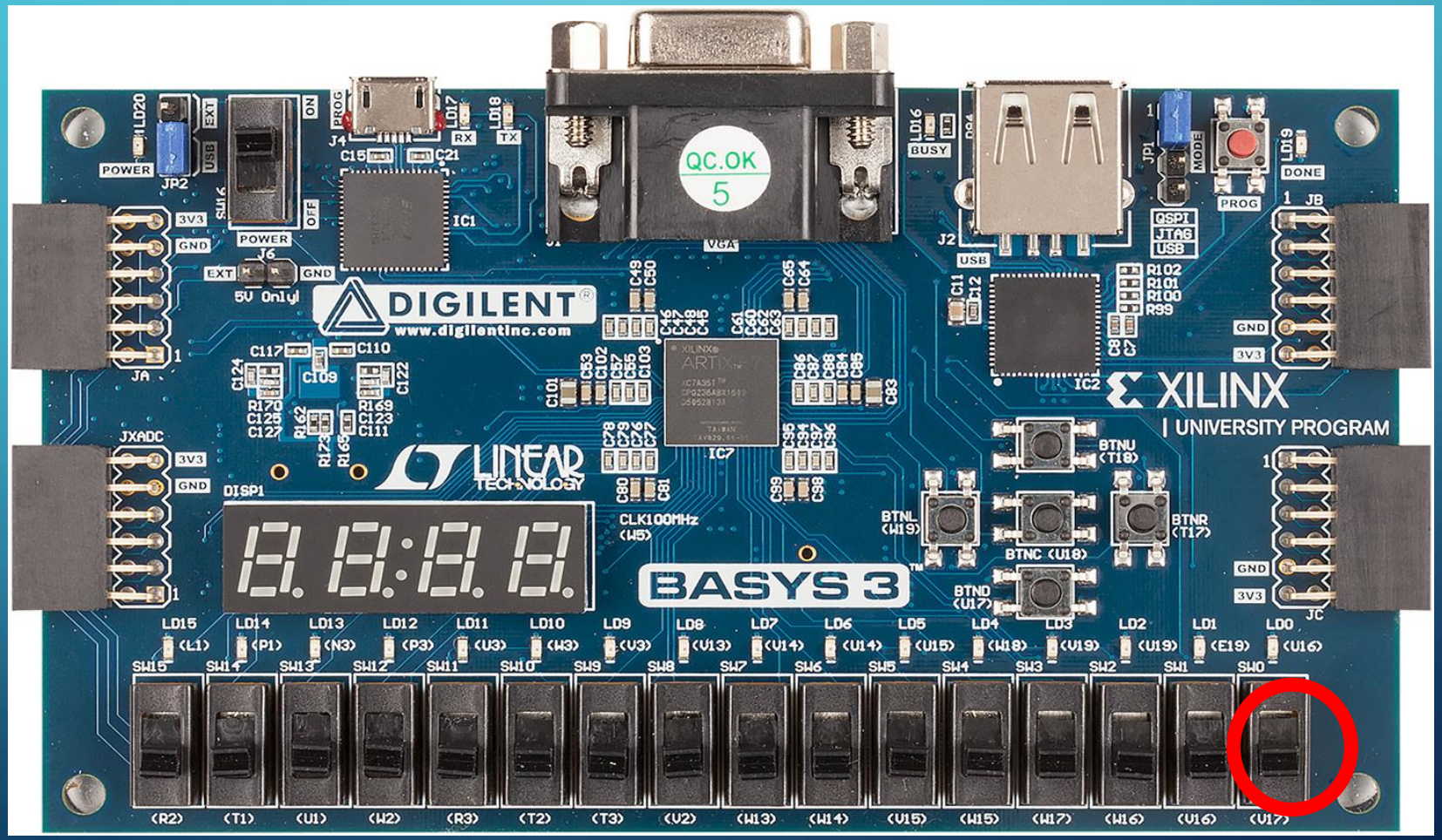

RESULT IN BINARY

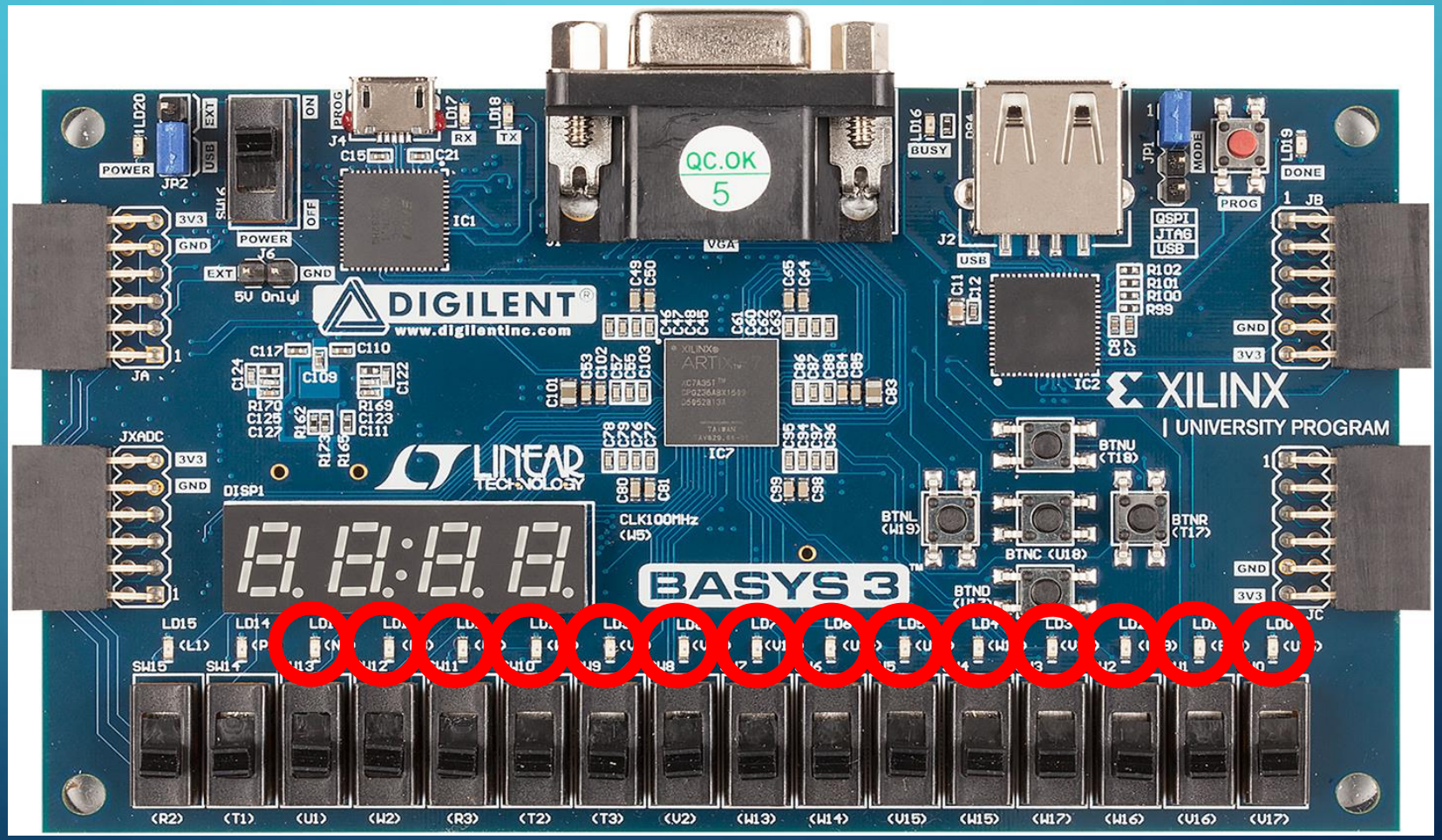

BLOCK DIAGRAM

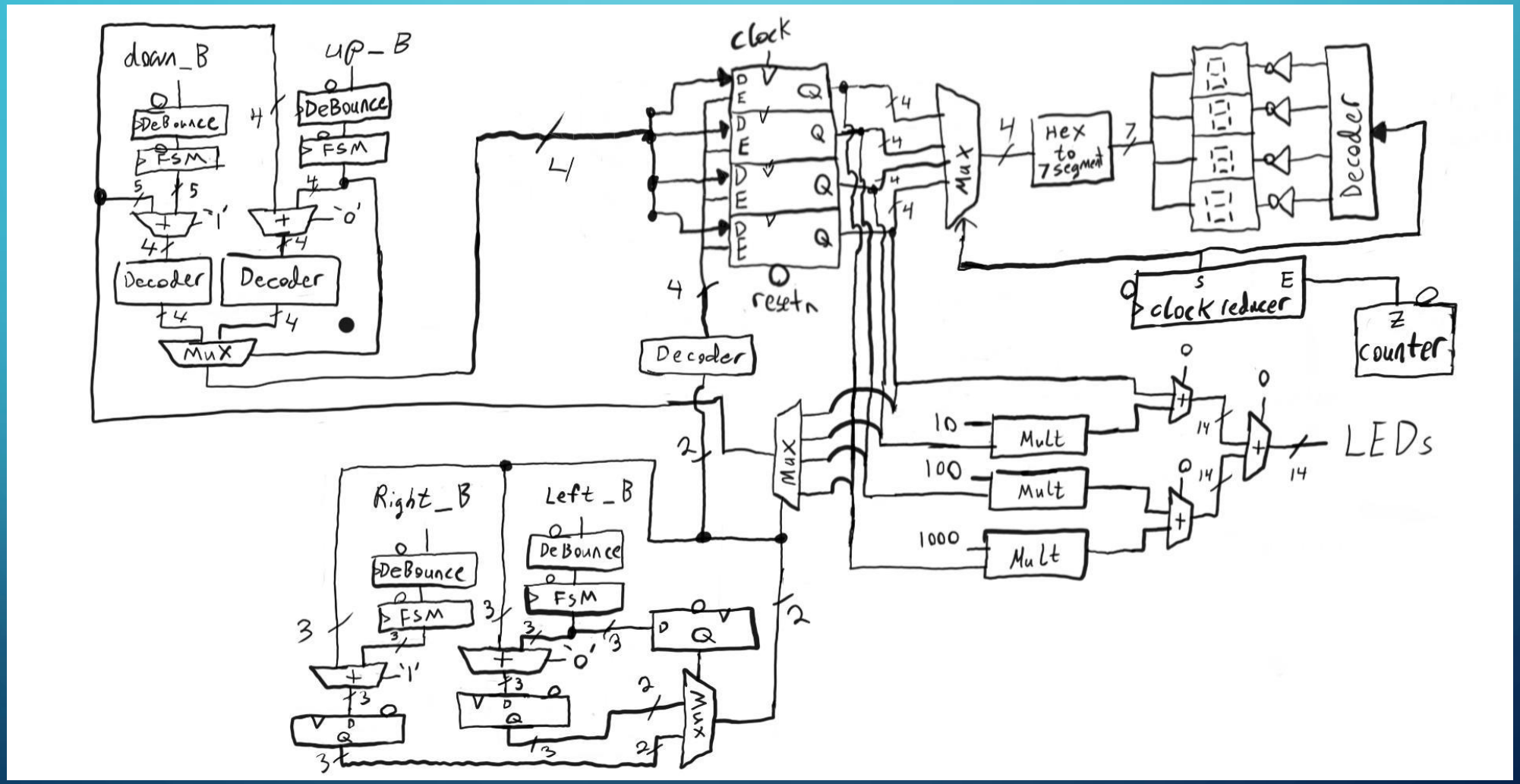

CLOCK REDUCER FSM

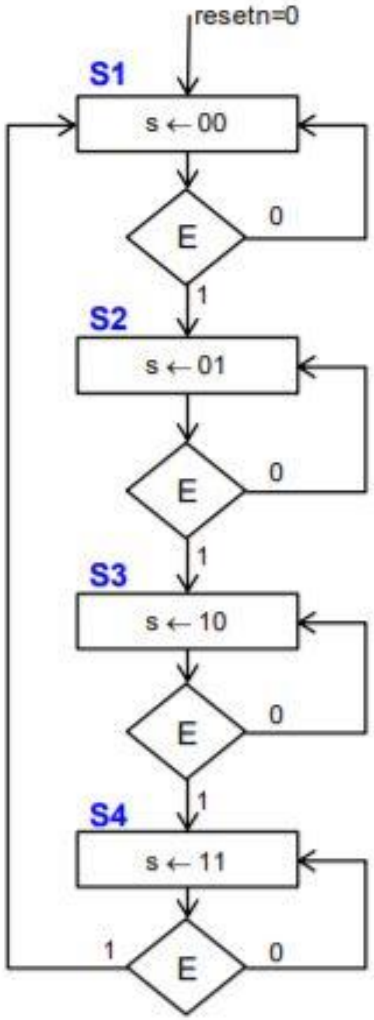

BUTTON REJECT FSM